

# SHIKSHA CLASSES

Subject: Physics

Question Paper

Class : XI 11 : Electric Current Through Conductors Time : 1 Hour

4

## **SECTION-A**

## Q.1 : Choose the correct option :

- i) A current of 1.6 A is passed through an electric lamp for half a minute. If the charge on the electron is  $1.6 \times 10^{-19}$  C, the number of electrons passing through it is -----.
  - a)  $1 \times 10^{19}$
- b)  $1.5 \times 10^{20}$
- c)  $3 \times 10^{19}$
- d)  $3 \times 10^{20}$
- ii) Which of the following is an ohmic conductor?
  - a) transistorelectrolyte
- b) vacuum tube c d) nichrome wire
- iii) Masses of three pieces of wires made of the same metal are in the ratio 1:3:5 and their lengths are in the ratio 5:3:1. The ratios of their resistances are
  - a) 1:3:5
- b) 5:3:1
- c) 1:15:125
- d) 125:15:1
- iv) You are given four bulbs of 25 W, 40 W, 60 W, and 100 W of power, all operating at 230 V. Which of them has the lowest resistance?
  - a) 25 W
- b) 40 W
- c) 60 W
- d) 100 W

# Q.2 : Answer the following:

- i) Define temperature coefficient of resistivity.
- ii) Define current.

#### **SECTION B**

- : Answer the following: (ANY 2) 4
- Q.3: Derive relation between current density and drift velocity.

Q.4 : How much work is done in moving a charge of 1.2 C from a point at 100 V to 180 V?

Total Marks :20

**Q.5**: Explain variation of resistivity with temperature.

#### **SECTION C**

- : Answer the following : (ANY 2)
- **Q.6**: Explain working of a circuit when connected to emf device.
- Q.7 : A metal wire of specific resistance  $64 \times 10^{-6} \Omega$  m and length 1.98 cm has a resistance of  $7\Omega$ . Find its radius.
- Q.8: Derive expression for potential energy when a charge flows through an external resistance in a circuit.

### **SECTION D**

- : Answer the following : (ANY 1)
- **Q.9**: A potential difference of 200 V is maintained across a conductor and current flowing through it is 2A. Find;
  - i) resistance and
  - ii) charge flowing through resistance for 15 seconds.
  - iii) the number of electrons flowing through the conductor in 15 seconds.
- **Q.10:** Explain parallel combination of resistors.

\* \* \*

